

A dark blue vertical bar on the left side of the slide. A blue arrow points to the right from the bar, containing the date.

3/11/2022

# Lab #6

UART receiver

Several thin, curved lines in dark blue and light grey originate from the bottom left and curve upwards and to the right.

Spence Johnston

CST 231 – DIGITAL SYSTEM DESIGN I

Spence Johnston

## Table of Contents

Abstract.....	2
Introduction .....	3
Design.....	3
Physical hardware design.....	3
Synthesized hardware design .....	3
Design Structure.....	4
.....	4
Modules .....	4
.....	6
Simulation and Testing.....	6
Problems .....	6
Results and Conclusion .....	7
Appendix .....	8
Table of Figures.....	9
References .....	10

## Abstract

The object of this lab is to receive input from a computer through UART communication. Once received, the character is displayed on the seven segment displays. It then casts lower case letter to uppercase, and outputs it back to the computer.

Two clock dividers were necessary for this lab. Both branch from the system clock. The transmitter needs to run at 9600 Baud. The receiver needs to run at 16 times this speed. There is a manual switch, named reset. There is a UART input that is connected to the USB adapter. The transmit module outputs to the adapter. The seven segment displays on the development board were used to display the input.

The only issue I had with this lab was with timing. I was having an off by one error with my bounds when dealing with a slower clock speed.

Overall, I found this lab to be very educational. It has shown me how to interact with a computer using an embedded device. Although difficult, I found this lab to be very rewarding.

## Introduction

The object of this lab is to receive input from a computer through UART communication. Once received, the character is displayed on the seven segment displays. It then casts lower case letter to uppercase, and outputs it back to the computer.

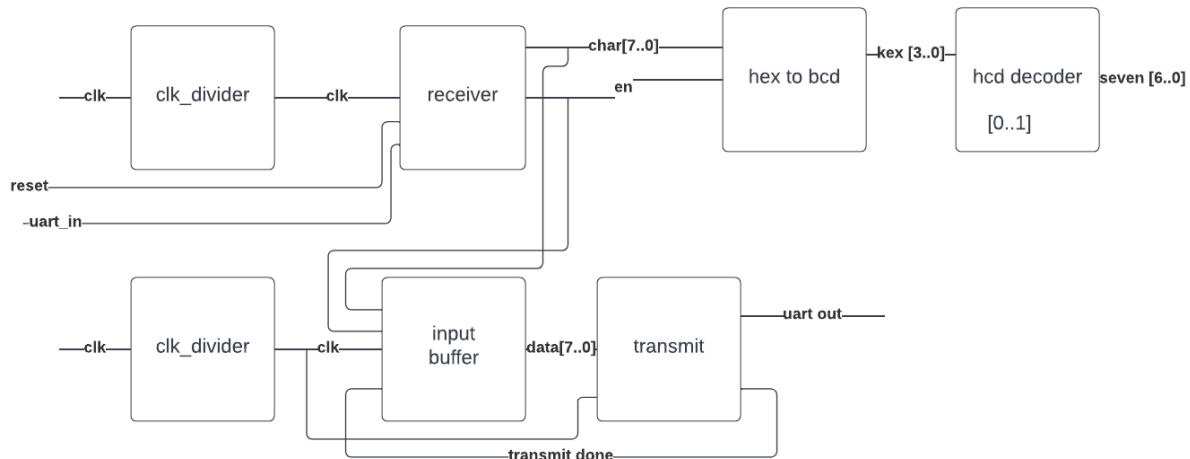


Figure 1: Block diagram

## Design

### Physical hardware design

The hardware used for this lab was the development board Cyclone V and a USB to UART adapter. No other components were necessary. The board was connected to the adapter via the GPIO pins. One connects to the adapters Rx and Tx cables. A common ground is necessary for reference voltages.

 


Figure 2: wiring schematic

### Synthesized hardware design

Two clock dividers were necessary for this lab. Both branch from the system clock. The transmitter needs to run at 9600 Baud. The receiver needs to run at 16 times this speed. There is a manual switch,

named reset. There is a UART input that is connected to the USB adapter. The transmit module outputs to the adapter. The seven segment displays on the development board were used to display the input.

## Design Structure

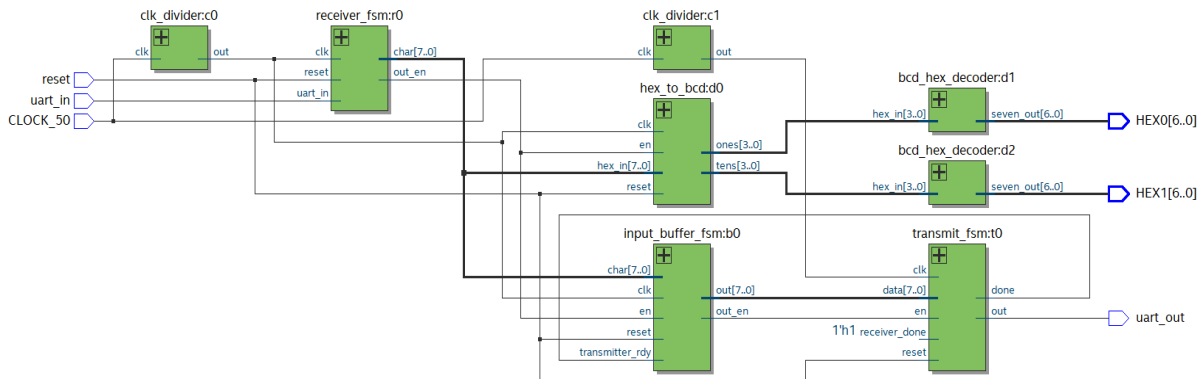


Figure 3: Top level RTL

## Modules

### Clk\_divider

Accepts the system clock. Outputs a slower clock. Two used for this lab. One for the receiver and one for the transmitter. Receiver set to 16 times the Baud rate. See previous labs for further details.

### Receiver\_fsm

Accepts UART communication. Runs at 16 times the transmitter speed. Polls for data on the eighth pulse. Outputs the character once the data is received. Sends an enable signal. As shown below, the data gets collected then it sends a enable signal via the SEND state.

 


Figure 4: receiver\_fsm state diagram

### Hex\_to\_bcd

This module breaks up the value from receiver for seven segment display. Similar to bcd, but for hex. On enable, the state changes to CHANGE. This changes the values on the seven-segment display.

 


Figure 5:hex\_to\_bcd state diagram

#### *Bcd\_hex\_decoder*

This decodes a binary coded hex and outputs the appropriate seven segment display output.

#### *Input\_buffer\_fsm*

This module is the buffer between the clock domains. It stores the input and releases it to the transmitter.

 


Figure 6: input\_buffer\_fsm state diagram

#### *Transmit\_fsm*

This module handles the UART communication. This accepts an enable and a character. It wraps the data in the UART specifications, and outputs it serially.

 


Figure 7: transmit state machine

## Simulation and Testing

 


Figure 8: transmit simulation

 


Figure 9: receiver simulation

 


Figure 10: hex\_to\_bcd simulation

## Problems

The only issue I had with this lab was with timing. I was having an off by one error with my bounds when dealing with a slower clock speed.

## Results and Conclusion

Overall, I found this lab to be very educational. It has shown me how to interact with a computer using an embedded device. Although difficult, I found this lab to be very rewarding.



## Appendix

in	CLOCK_50	Input	PIN_AF14	3B	B3B_NO	3.3-V LVTTTL	16mA ...ault)	
out	HEX0[6]	Output	PIN_AH28	5A	B5A_NO	3.3-V LVTTTL	16mA ...ault)	1 (default)
out	HEX0[5]	Output	PIN_AG28	5A	B5A_NO	3.3-V LVTTTL	16mA ...ault)	1 (default)
out	HEX0[4]	Output	PIN_AF28	5A	B5A_NO	3.3-V LVTTTL	16mA ...ault)	1 (default)
out	HEX0[3]	Output	PIN_AG27	5A	B5A_NO	3.3-V LVTTTL	16mA ...ault)	1 (default)
out	HEX0[2]	Output	PIN_AE28	5A	B5A_NO	3.3-V LVTTTL	16mA ...ault)	1 (default)
out	HEX0[1]	Output	PIN_AE27	5A	B5A_NO	3.3-V LVTTTL	16mA ...ault)	1 (default)
out	HEX0[0]	Output	PIN_AE26	5A	B5A_NO	3.3-V LVTTTL	16mA ...ault)	1 (default)
out	HEX1[6]	Output	PIN_AD27	5A	B5A_NO	3.3-V LVTTTL	16mA ...ault)	1 (default)
out	HEX1[5]	Output	PIN_AF30	5A	B5A_NO	3.3-V LVTTTL	16mA ...ault)	1 (default)
out	HEX1[4]	Output	PIN_AF29	5A	B5A_NO	3.3-V LVTTTL	16mA ...ault)	1 (default)
out	HEX1[3]	Output	PIN_AG30	5A	B5A_NO	3.3-V LVTTTL	16mA ...ault)	1 (default)
out	HEX1[2]	Output	PIN_AH30	5A	B5A_NO	3.3-V LVTTTL	16mA ...ault)	1 (default)
out	HEX1[1]	Output	PIN_AH29	5A	B5A_NO	3.3-V LVTTTL	16mA ...ault)	1 (default)
out	HEX1[0]	Output	PIN_AJ29	5A	B5A_NO	3.3-V LVTTTL	16mA ...ault)	1 (default)
in	reset	Input	PIN_AB12	3A	B3A_NO	3.3-V LVTTTL	16mA ...ault)	
in	uart_in	Input	PIN_Y17	4A	B4A_NO	3.3-V LVTTTL	16mA ...ault)	
out	uart_out	Output	PIN_Y18	4A	B4A_NO	3.3-V LVTTTL	16mA ...ault)	1 (default)

Figure 11: pinout

## Table of Figures

Figure 1: Block diagram.....	3
Figure 2: wiring schematic .....	3
Figure 3: Top level RTL .....	4
Figure 4: receiver_fsm state diagram .....	4
Figure 5:hex_to_bcd state diagram .....	5
Figure 6: input_buffer_fsm state diagram.....	5
Figure 7: transmit state machine .....	6
Figure 8: transmit simulation.....	6
Figure 9: receiver simulation .....	6
Figure 10: hex_to_bcd simulation .....	6
Figure 11: pinout.....	8

## References

There are no sources in the current document.